

A Direct Digital Synthesizer with Arbitrary Modulus

Suppose you have a system with a 10 MHz sample clock, and you want to generate a sampled sinewave at any frequency below 5 MHz on 500 kHz spacing; i.e., 0.5, 1.0, 1.5, ... MHz. In other words, $f = k \cdot f_s / 20$, where k is an integer and f_s is sample frequency. This article shows how to do this using a simple Direct Digital Synthesizer (DDS) with a look-up table that is at most 20 entries long. We'll also demonstrate a Quadrature-output DDS. A note on terminology: some authors call a DDS a Numerically-Controlled Oscillator (NCO).

Disclaimer: I have not implemented this DDS in hardware, so there could be problems with the scheme that I have not anticipated.

Background [1,2]

A continuous-time sinewave with frequency f_0 is given by $y = \sin(2\pi f_0 t + \phi_0)$. For a sampled signal, we replace t by nT_s , where n is the sample number and T_s is the sample time. Letting $\phi_0 = 0$, we have:

$$y = \sin(2\pi f_0 n T_s)$$

The phase of the signal is:

$$\Phi = 2\pi f_0 n T_s \quad \text{rad (mod } 2\pi),$$

Or

$$\Phi = f_0 n T_s \quad \text{cycles (mod 1)} \quad (1)$$

The phase wraps every 2π radians = 1 cycle. Equation 1 shows that the phase increases (accumulates) by $f_0 T_s$ every sample. So we can calculate the phase using an accumulator with input = $f_0 T_s$, as shown in Figure 1a. The value of ϕ has a range of 0 to 1 (cycles). We generate the sinewave from the phase using a look-up table (LUT). What we've just described is a basic DDS. Note that another option to generate the sinewave from the phase not discussed here is the CORDIC algorithm [3].


Figure 1b adds quantization in the accumulator register, the phase, and the LUT entries. The accumulator input has 2^C steps over a range of 0 to 1, giving a frequency step $\Delta f = f_s / 2^C$, where f_s is the sample frequency. The resulting output frequencies are $f_s / 2^C, 2f_s / 2^C, 3f_s / 2^C \dots$. Given the 2^C steps, we can say the DDS has a modulus of 2^C . As an example, if $C = 24$ bits, and $f_s = 10$ MHz, the frequency step is:

$$\Delta f = 10\text{E}6 / 2^{24} = 0.59605 \text{ Hz.}$$


This frequency step is impressively small. However, if you want to program a frequency that is not on one of the steps, such as $f_s / 10$, there will be a small frequency error of up to $\Delta f / 2$.

If we were to maintain the 24 bits of phase, the LUT size for this example, taking symmetry of the sine into account, would be $\frac{1}{4} * 2^{24} = 2^{22} = 4,194,304$ entries. To avoid such a large LUT, the phase is normally quantized to $P < C$ bits. The phase quantization results in so-called phase truncation spurs in the output spectrum. A typical value of P used in DDS chips is 15 bits, which, taking advantage of the symmetry of the sine, gives LUT size of $2^{13} = 8192$ entries.

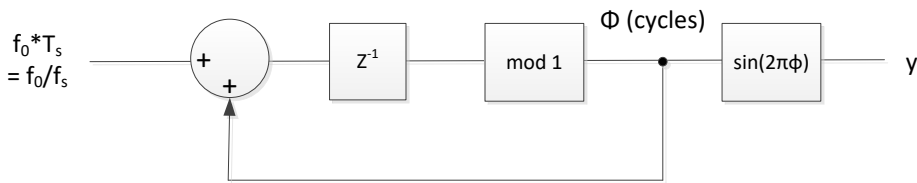You can see that a standard DDS is not a perfect solution to our problem of generating $f_0 = k * f_s / 20$: it does not produce the exact frequency; it requires a not-so-small LUT; and it has spurs due to truncation of the phase. (Note that there are techniques for reducing phase-truncation spurs [4]).



(a)

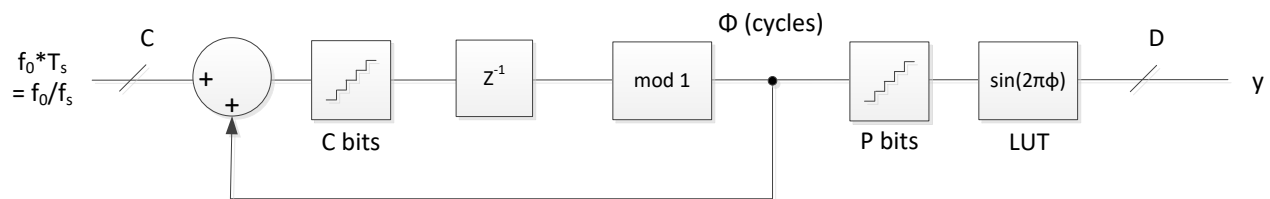

(b)

Figure 1. a) Implementation of Equation 1. b) DDS with quantization.

DDS with Arbitrary Modulus

A DDS with modulus other than 2^C can address the shortcomings of a conventional DDS for our application.

If we multiply both sides of Equation 1 by an integer L , we get:

$$L\Phi = Lf_0nT_s \pmod{L}$$

This equation can be implemented by modifying the accumulator in Figure 1a as shown in Figure 2. Here we require m to be an integer between 0 and $L-1$, so there are L entries in the LUT, where L is not restricted to 2^C . The input $L*f_0/fs$ is an integer:

$$L*f_0/fs = k \quad (2)$$

or $f_0 = k*fs/L \quad (3)$

Since k is an integer, f_0 has a step size of $\Delta f = fs/L$. For a given Δf and fs , we have:

$$L = fs/\Delta f \quad (4)$$

Letting $f_s = 10$ MHz and $\Delta f = 0.5$ MHz, we get $L = 20$. The number of bits required for the accumulator is found by taking $\log_2(L)$ and rounding up to the next integer. For $L = 20$, we need 5 bits.

As shown in Figure 2, $m = L\phi$, so the phase is $\phi = m/L$. Simplistically, the LUT entries are:

$$u(m) = \sin(2\pi m/L), \quad m = 0: L-1 \quad (5)$$

However, for fixed point entries, we need to round the values of $u(m)$ and prevent overflow when $m = L/4$ and $u(L/4) = \sin(\pi/2) = 1.0$. (For example, if the number of bits $D = 8$, the largest allowable entry is not 1.0 but $(2^7 - 1)/2^7 = 127/128 = 01111111$). We can compute the fixed-point entries as:

$$\begin{aligned} u(m) &= (1 - \epsilon) * \sin(2\pi m/L), \quad m = 0: L-1 \\ \text{LUT}(m) &= \text{round}(u(m)*2^{D-1})/2^{D-1} \end{aligned} \quad (6),$$

Where D is the number of bits in the 2's complement LUT entry and $\epsilon \ll 1$. I used $\epsilon = 1/2^{D-2}$. Multiplication by $1 - \epsilon$ makes the LUT entry for $m = L/4$ less than 1.0 after rounding.

For our case, with $L = 20$, the LUT values are plotted in figure 3. The LUT contains one cycle of a sinewave evaluated over L samples. Note that when L is a multiple of 4, it is possible to reduce the LUT size to $L/4$ entries by taking the symmetry of the sinewave into account.

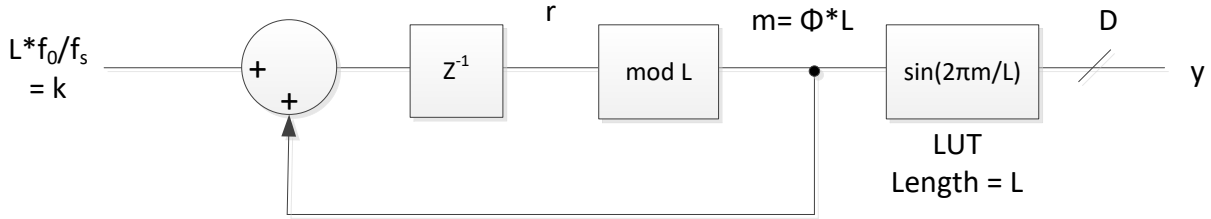


Figure 2. DDS with arbitrary modulus

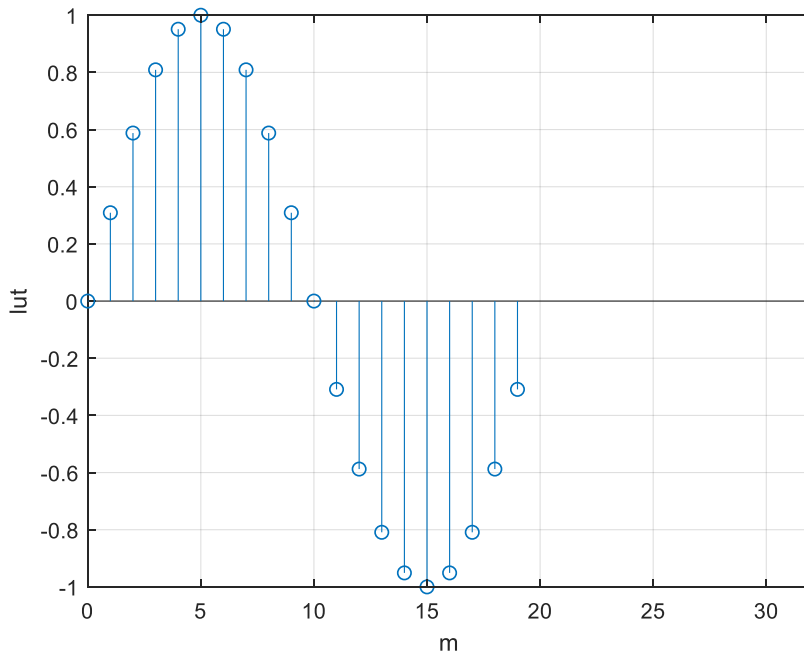


Figure 3. Sine look-up table for L= 20

Let's look at the behavior of our example DDS, with $f_s = 10$ Hz and $\Delta f = 0.5$ Hz. The Matlab code is listed in the Appendix. To start out, let the output frequency $f_0 = 0.5$ Hz. From equations 2 and 4, $k = f_0/\Delta f$, so $k = 1$. As shown in Figure 4, m increments through all the integers from 0 to $L-1$, then repeats. So the DDS just steps through every entry of the LUT. Also shown in Figure 4 is the phase $\phi = m/L$ cycles, and the sampled sinewave output.

Now, if we let $f_0 = 1$ Hz, $k = 2$. Thus $m = 0, 2, 4, \dots$ and the DDS steps through every 2nd entry of the LUT, as shown in Figures 5a and 5b.

If we let $f_0 = 1.5$ Hz, $k = 3$. Thus $m = 0, 3, 6, \dots$ and the DDS steps through every 3rd entry of the LUT, as shown in Figures 5c and 5d. As can be seen in Figure 5c, it takes three cycles for the phase sequence to repeat.

For $L = 20$, the allowable output frequencies f_0 that are less than $f_s/2$ are: 0.5, 1, 1.5, 2, 2.5, 3, 3.5, 4, and 4.5 Hz, corresponding to $k = 1: 9$. For L even, there are $L/2 - 1$ allowable values of f_0 .

Since accumulator output m is always an integer, there is no phase truncation error. The only error in the output y is due to rounding of the LUT entries. Figure 6 compares spectra for $f_0 = 1.5$ Hz of a conventional DDS with 15-bits of phase to our DDS with $L = 20$ (4.3 bits of phase). Both have 16-bit LUT entries. The modulus 20 DDS has lower spurious, with the worst spur at about -105 dB with respect to the level at 1.5 Hz.

Finally, note that it is also possible to make a DDS with an arbitrary *programmable* modulus. The approach involves using two accumulators [5,6].

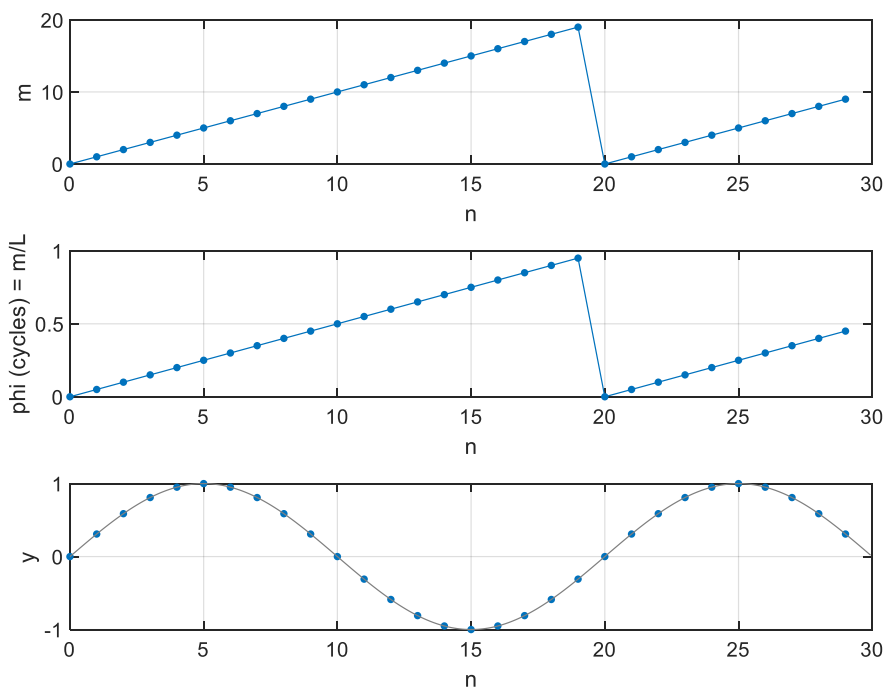


Figure 4. DDS with $L = 20$ and $f_s = 10$ Hz.

a) Accumulator output m for $f_0 = 0.5$ Hz. b) Phase in cycles. c) LUT output y .

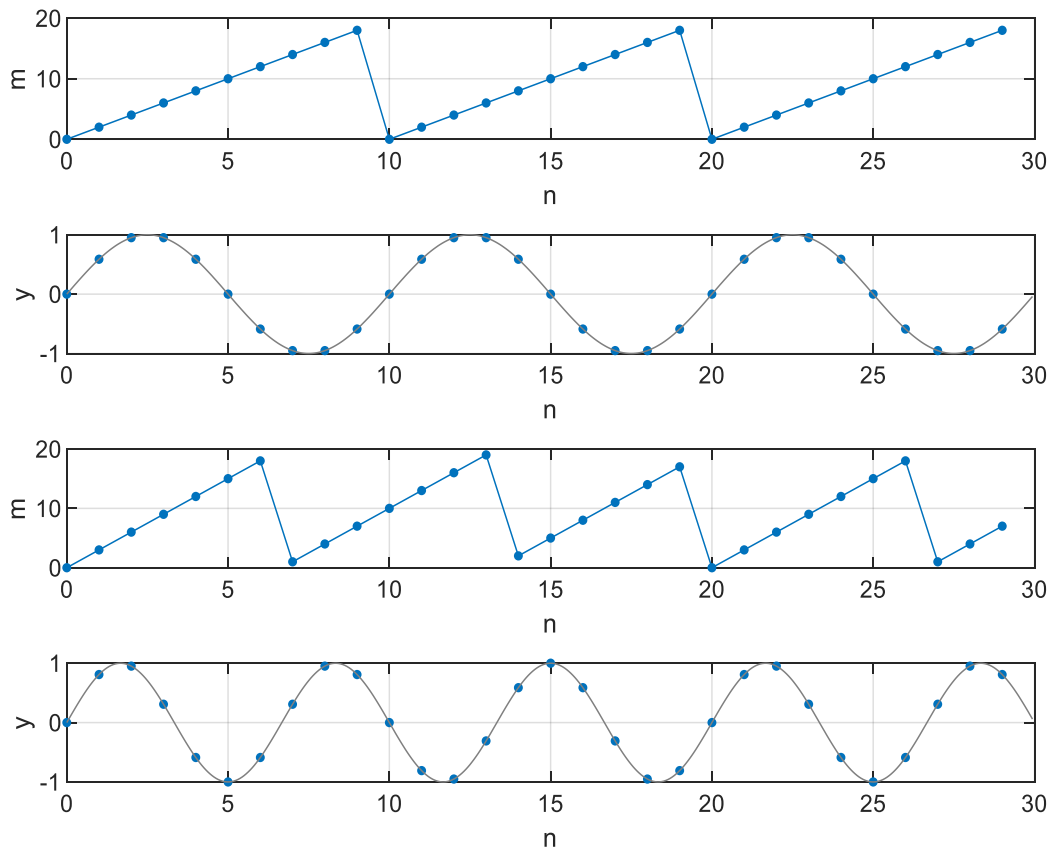


Figure 5. DDS with $L = 20$ and $f_s = 10$ Hz.

- a) Accumulator output m for $f_0 = 1.0$ Hz, and
- b) LUT output y
- c) Accumulator output m for $f_0 = 1.5$ Hz, and
- d) LUT output y

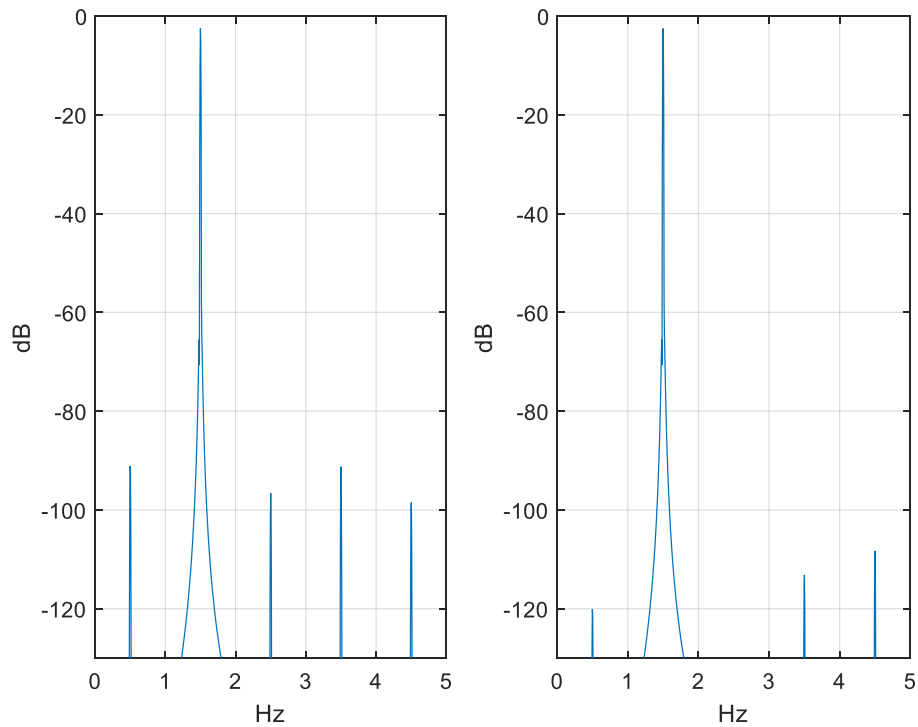


Figure 6. Spectra of conventional DDS and DDS with modulus $L=20$. $f_0 = 1.5$ Hz and $f_s = 10$ Hz.
 Left: Conventional DDS with 15 bits of phase and 16-bit LUT entries.
 Right: DDS with $L=20$ (4.3 bits of phase) and 16-bit LUT entries.

Quadrature Output DDS

A quadrature output DDS has both cosine and -sine outputs. The cosine phase leads sine phase by $\pi/2$ radians = $\frac{1}{4}$ cycle. Given m as the LUT address for a sine, the address for the cosine is:

$$p = m + L/4 \pmod{L}$$

where L is the DDS modulus = LUT length, which must be a multiple of 4. We can modify the Matlab code in the Appendix to compute both sine and cosine. Here is the modified *for* loop:

```
sine(1)= 0;
cosine(1)= 1;
m= 0;
for n= 2:N
    r = k + m;
    m= mod(r,L);
    p= mod(m+ L/4,L);
    sine(n)= lut(m+1);
    cosine(n)= lut(p+1);
end
```

% LUT address/ sine
 % LUT address/ cosine
 % sine output
 % cosine output

The Quadrature DDS outputs for $L= 20$, $f_s= 10$ Hz, and $f_0 = 1$ Hz are shown in Figure 7.

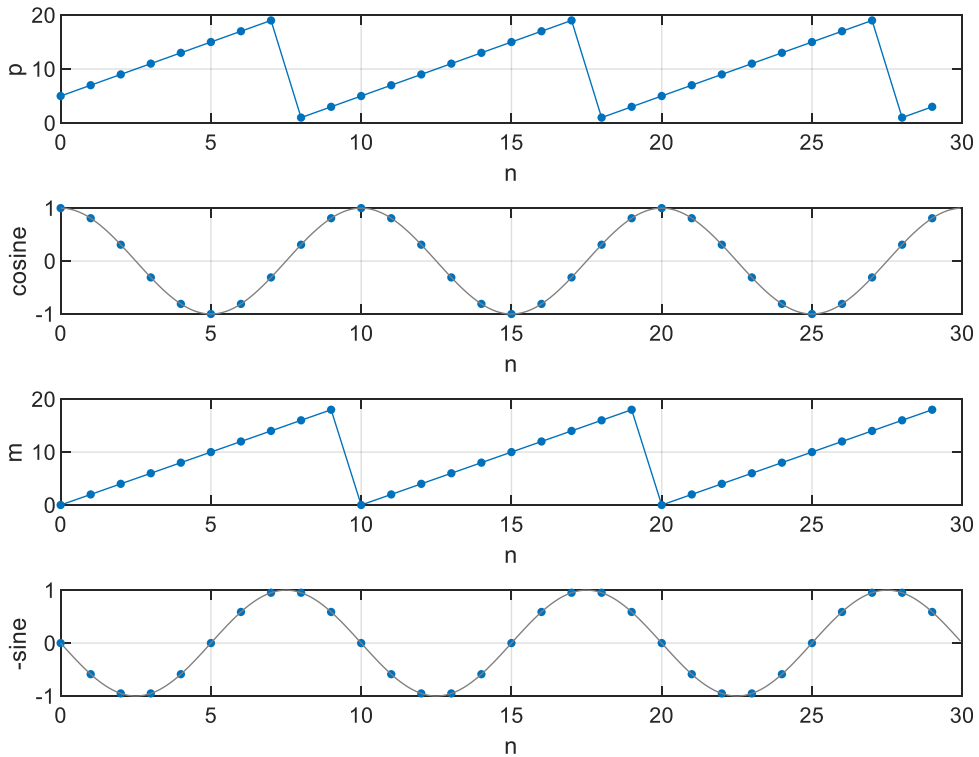


Figure 7. Quadrature DDS with $L= 20$, $f_s = 10$ Hz, and $f_0 = 1$ Hz.

- a) cosine address p. b) cosine output. c) sine address m. d) -sine output.

Simplest DDS with $L= 4$

If we let $L= 4$, there is only one output frequency below $f_s/2$:

$$f_0 = k \cdot f_s / L = f_s / 4 \quad (k= 1)$$

The LUT sine values from Equation 5 are:

$$\begin{aligned} \text{LUT} &= [0 \sin(\pi/2) 0 \sin(3\pi/2)] \\ &= [0 1 0 -1] \end{aligned}$$

The cosine values are $[1 0 -1 0]$.

A quadrature $L=4$ DDS using cosine and -sine can be used to down-convert a signal centered at $f_s/4$ to complex baseband [7,8]. Since all LUT values are 0 or +/-1, no multiplier is needed to perform the frequency conversion.

References

1. MT-085, "Fundamentals of Direct Digital Synthesis (DDS)", Analog Devices, 2009, <https://www.analog.com/media/en/training-seminars/tutorials/MT-085.pdf>
2. "A Technical Tutorial on Digital Signal Synthesis", Analog Devices, 1999, https://www.analog.com/media/cn/training-seminars/tutorials/450968421DDS_Tutorial_rev12-2-99.pdf
3. Rice, Michael, Digital Communications, A Discrete-Time Approach, Pearson, 2009, section 9.4.
4. Rice, section 9.2.
5. Gentile, Ken, AN-953, "Direct Digital Synthesis with a Programmable Modulus", Analog Devices, 2014, <https://www.analog.com/media/en/technical-documentation/application-notes/AN-953.pdf>
6. Hou, Yuqing, et. al., "An Accurate DDS Method Using Compound Frequency Tuning Word and Its FPGA Implementation", *Electronics*, Nov, 2018, <https://www.mdpi.com/2079-9292/7/11/330>
7. Harris, Fredric J., Multirate Signal Processing, Prentice-Hall PTR, 2004, section 13.2.1.
8. Lyons, Richard G., Understanding Digital Signal Processing, 3rd Ed., Prentice-Hall, 2011, section 13.1.2.

Neil Robertson June 3, 2019. Revised 6/8/19

Appendix Matlab Code for DDS with Modulus = 20

```
% dds_mod20.m 5/30/19 Neil Robertson
% DDS with modulus L = 20
% output frequency f0 = k*fs/L
% Plot LUT, phase, and output

fs= 10;           % Hz sample freq
df= 0.5;         % Hz desired freq step
L= fs/df         % length of LUT= modulus of accumulator

if mod(L,1)~=0
    error(' fs/fstep must be an integer')
end

% create LUT with one full cycle of sinewave (not using symmetry)
D= 16;           % bits LUT entries quantization
m= 0:L-1;
phi_lut= m/L;   % cycles phase
epsilon= 1/2^(D-2);
u= (1 - epsilon) *sin(2*pi*phi_lut);
lut= round(u*2^(D-1))/(2^(D-1)); % quantize lut entries
%
% DDS
N= 30;           % number of output samples
f0= 0.5;         % Hz output frequency (must be multiple of df)
k= L*f0/fs;     % integer input to DDS

y(1)= 0;
m= 0;
for n= 2:N
    r = k + m;
    m= mod(r,L); % LUT address
    y(n)= lut(m+1); % output
    phi(n)= m/L; % cycles phase
end
%
%
% Plotting
%
% plot LUT
stem(0:L-1,lut),grid
axis([0 32 -1 1])
xlabel('m'),ylabel('lut'),figure
%
%plot m and phi
subplot(311),plot(0:N-1,phi*L,'.-','markersize',9),grid
axis([0 N 0 20])
xlabel('n'),ylabel('m')
subplot(312),plot(0:N-1,phi,'.-','markersize',9),grid
axis([0 N 0 1])
xlabel('n'),ylabel('phi (cycles) = m/L')
%
```

```
% plot y along with "continuous" sinewave y2 in grey

fs_plot= fs*16;           % fs of "continuous" sine
Ts= 1/fs_plot;
Len= 16*N;
i= 0:Len-1;

y2= sin(2*pi*f0*i*Ts);    % "continuous" sine

subplot(313),plot(0:N-1,y, '.', 'markersize', 9),grid
hold on
plot(i/16,y2, 'color', [.5 .5 .5])
axis([0 N -1 1])
xlabel('n'),ylabel('y')
```